

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	24/07/2025	Batch No:	B2
Faculty Name:	Ms. Poonam Bhogle	Roll No:	16010124107
Faculty Sign & Date:		Grade/Marks:	31/07/25

Experiment No: 2

Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:
To implement half and full adder–subtractor using gates and IC 7483

COs to be achieved:
CO2: Use different minimization techniques and solve combinational circuits.

Tools used:
Trainer kits

Theory:
<p>Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:</p> <ul style="list-style-type: none"> • Half adder • Full adder <p>Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.</p> <p>Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.</p> <p>Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer .there are two types of subtractors:</p> <ul style="list-style-type: none"> • Half subtractor

- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.


2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no.

e.g. 2's complement of $+(10)_{10} = 1010$ is


1C of	01
1010	01
	+ 1
	01
-(10) ₁₀	10

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.

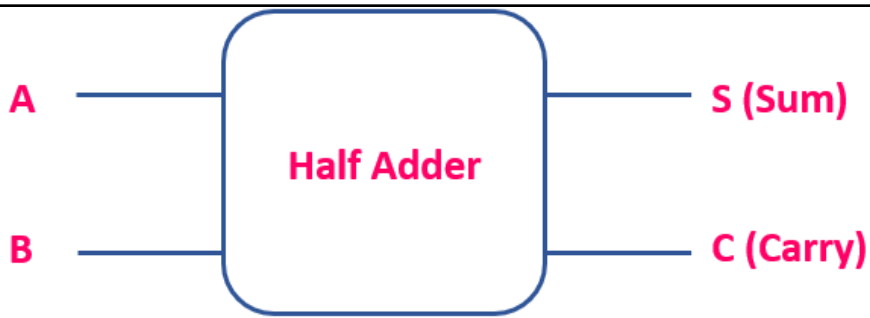Implementation Details: Half Adder Block Diagram



Half Adder Circuit

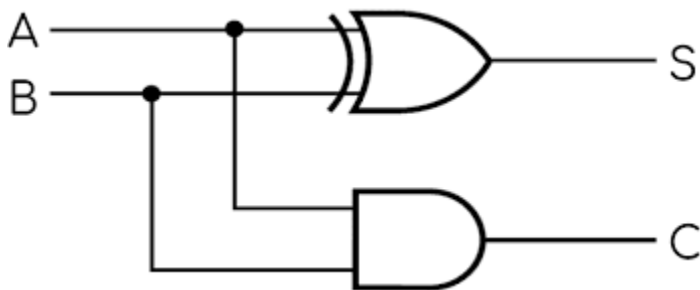



Truth Table for Half Adder

Inputs		Outputs	
A	B	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


From the truth table (with steps):

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1


Truth table

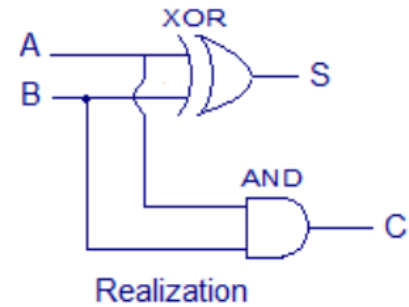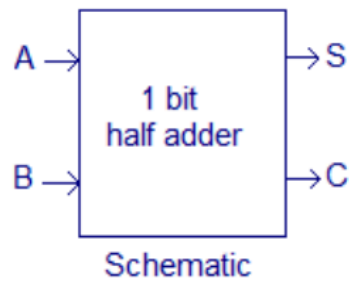

Full Adder Block Diagram

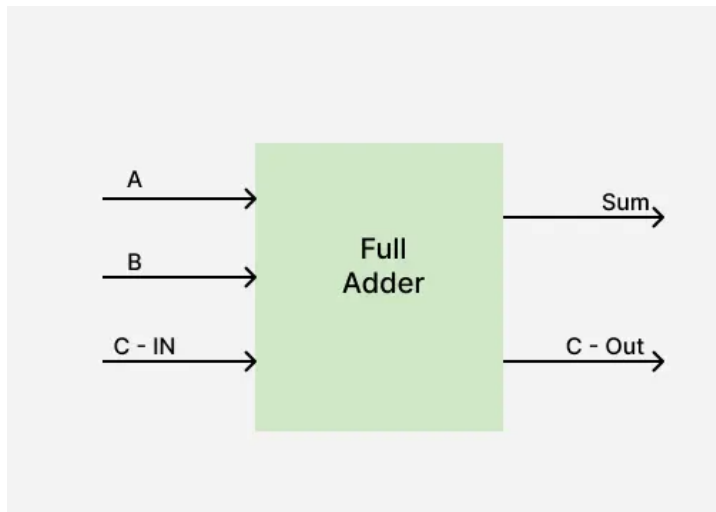

Full Adder Circuit

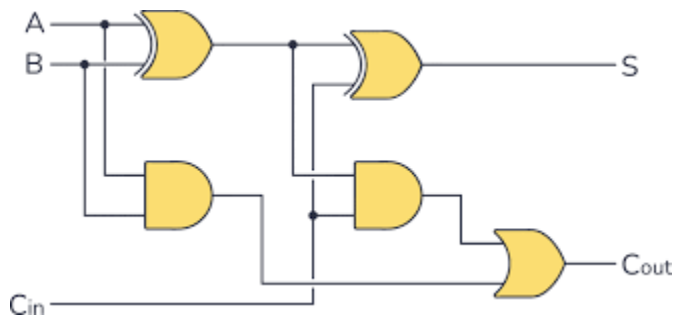


Truth Table for Full Adder


A	B	Cin	Sum (S)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From the truth table (with steps):


Full Adder Truth Table				
A	B	Cin	Cout	Sum
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

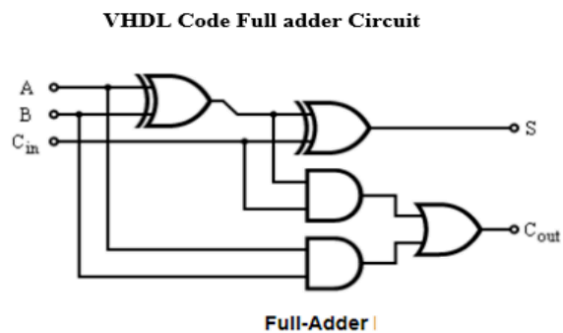

Half Subtractor Block Diagram

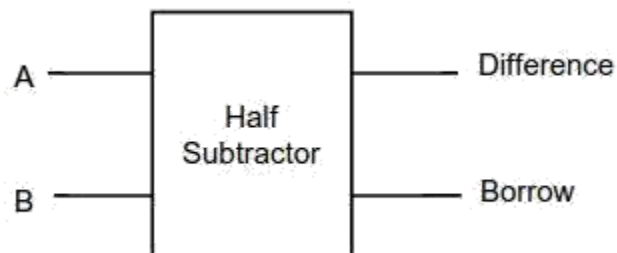

Half Subtractor Circuit


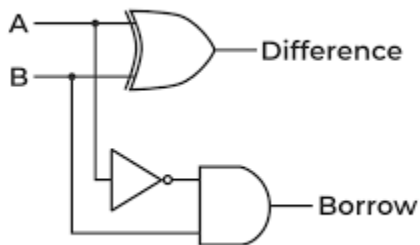


Truth Table for Half Subtractor


A	B	DIFFERENC E(D)	BORROW(B ₀)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

From the truth table (with steps) :


A	B	D	B ₀
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

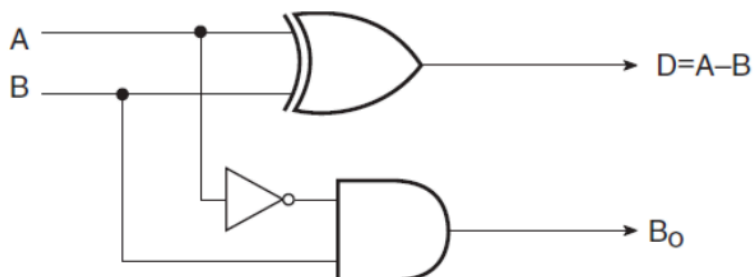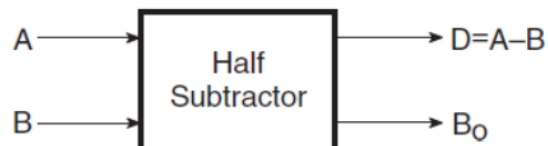

Full Subtractor Block Diagram

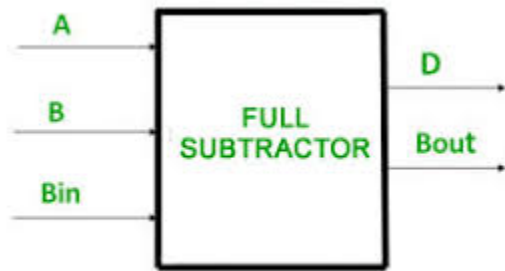

Full Subtractor Circuit

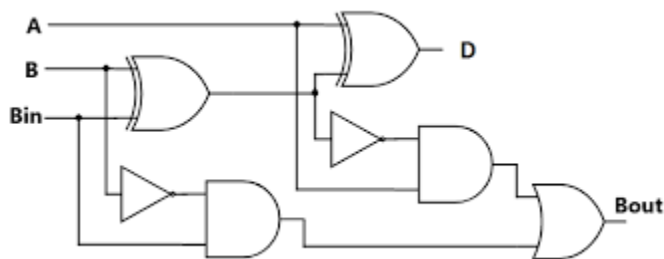

Truth Table for Full subtractor

A	B	B _{IN}	D	BOR _{OUT}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

$$\text{Differenc} = A'B'Bin + A'BBin' + AB'Bin' + ABBin$$

$$\text{Borrow out} = A'B + A'Bin + BBin$$

Input										Output	
A	B	Bin	$A \oplus B =$ C	$\sim A = E$	$E.B = F$	$Bin \oplus C = G$	$\sim C = F$	$F.Bin =$ H	$F + H = I$	D	Borr _{out}
0	0	0	0	1	0	0	1	0	1	0	0
0	0	1	0	1	0	1	1	1	1	1	1
0	1	0	1	1	1	1	0	0	0	1	1
0	1	1	1	1	1	0	0	0	0	0	1
1	0	0	1	0	0	1	0	0	0	1	0
1	0	1	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	1	0	0
1	1	1	0	0	0	1	1	1	1	1	1

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111


2 0010

1'C of 2
1101
+ 1


2'C of 2
1110

0111 + 1110 1
 0101


Pin Diagram IC7483

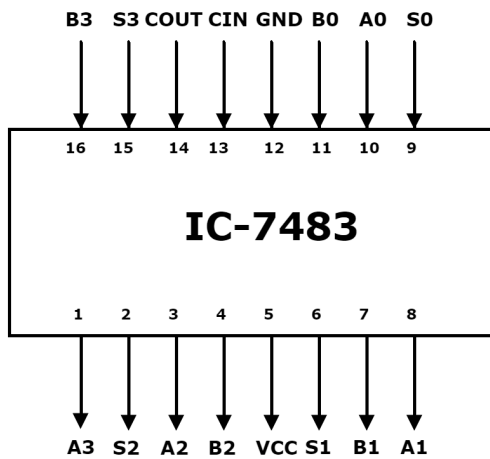

Adder

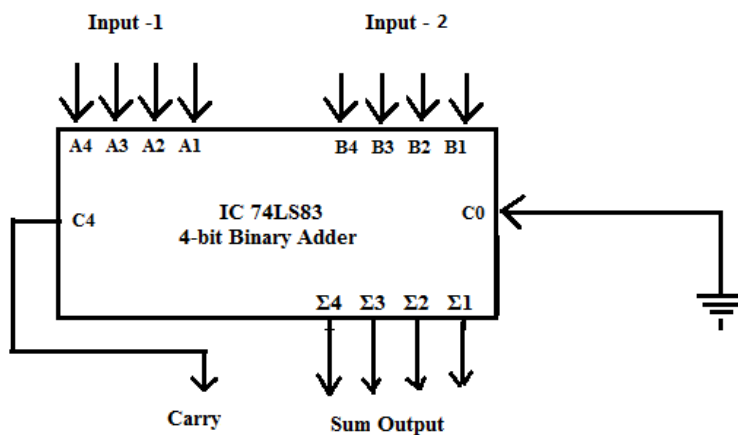

Subtractor

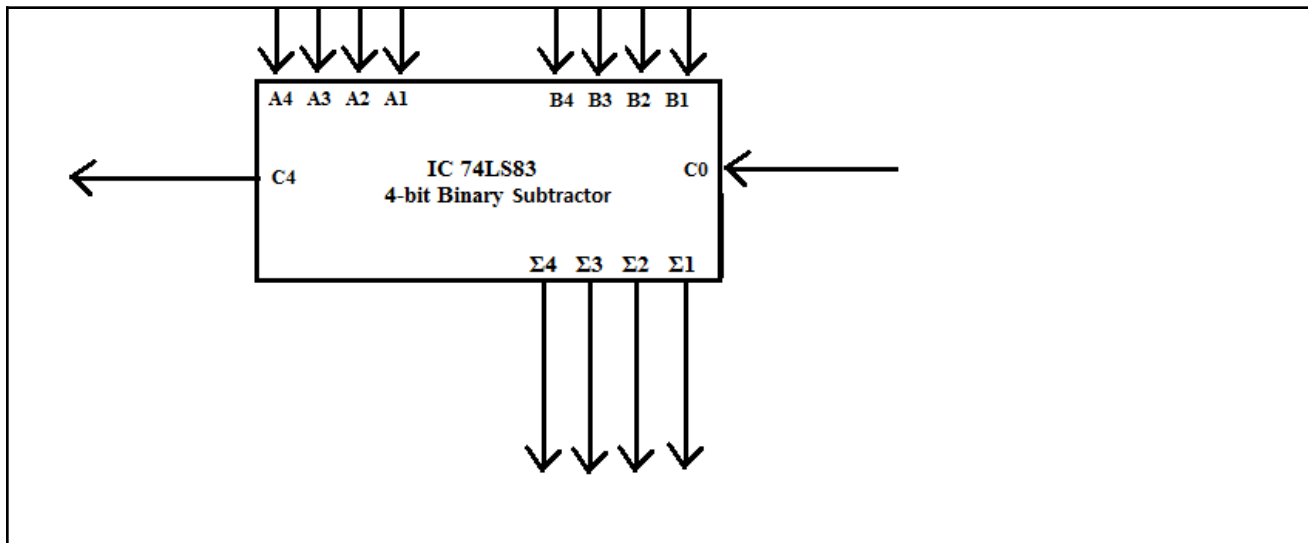


Implementation Details

Procedure:


- 1) Locate the IC 7483 and 4-not gates block on the trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

Post Lab Subjective/Objective type Questions:

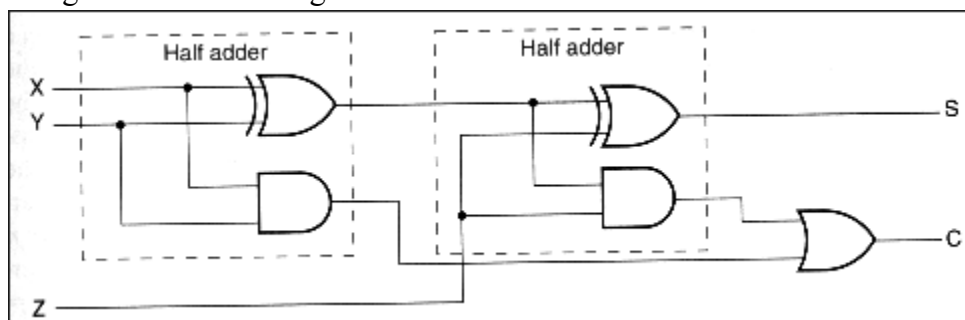
1. Design a full adder using two half adders.



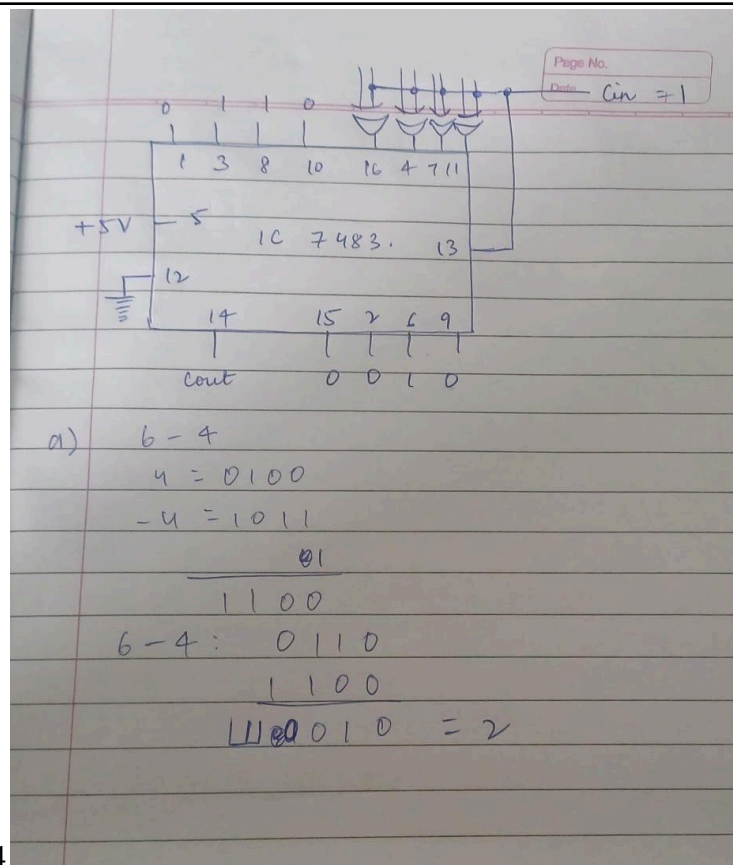2. Perform the following Binary subtraction with the help of appropriate ICs:



- a. 6-4
b. 5-8

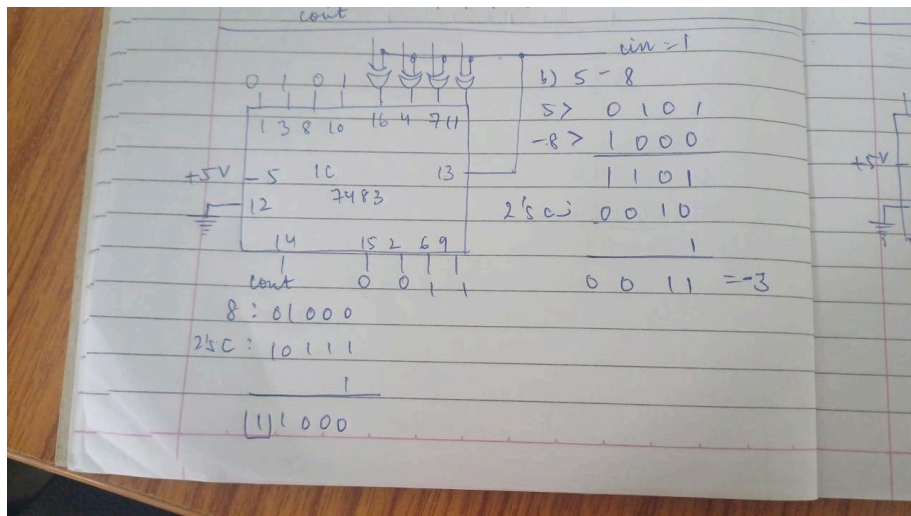

- c. 7-9

